

Name: _____ Period ____ Date: _____

Physics Lab: Foutan Board, Series and Parallel Circuits (CIPT)





Build various circuits, using a “Foutan Board” from Cornell University. Pomona College.

0. Optional board test: Insert switch plugs into 1 2 3 4 6 8 and 11. All four lamps should light.

1. Draw a circuit that has a battery, a test switch and a light bulb:



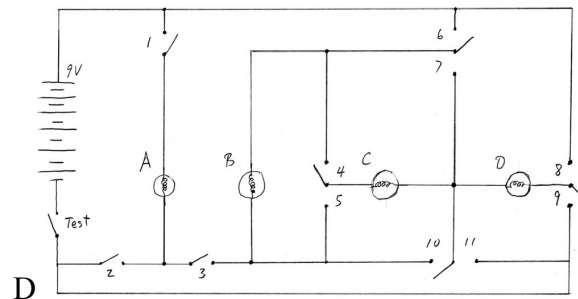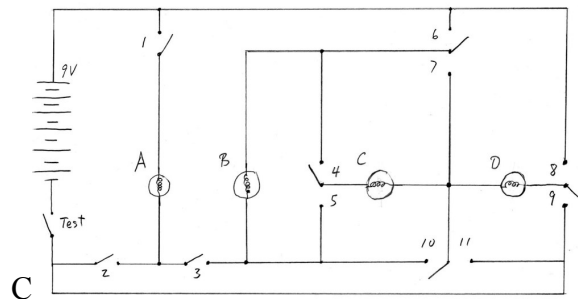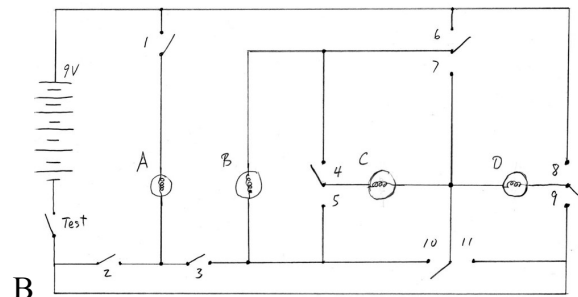
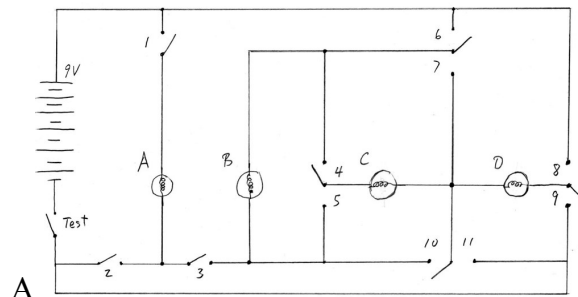
2. On the Foutan schematic, use a colored pencil to show how you would make this circuit using lamp A. Next, using lamp B, then C, then D.



3. Draw a circuit that has a battery, a test switch and two light bulbs in **series**.



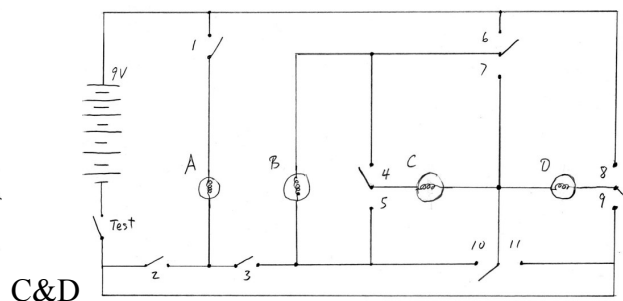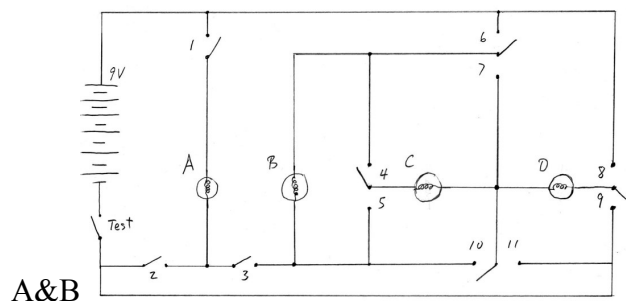
4. On the Foutan schematic, use a colored pencil to show how you would make this circuit using lamp A and B. Next, with C and D.




5. How can you test whether two lamps are in series? _____

6. What do you notice about the brightness of the bulbs?

 7. Draw a circuit that has a battery, a test switch and two light bulbs in **parallel**.



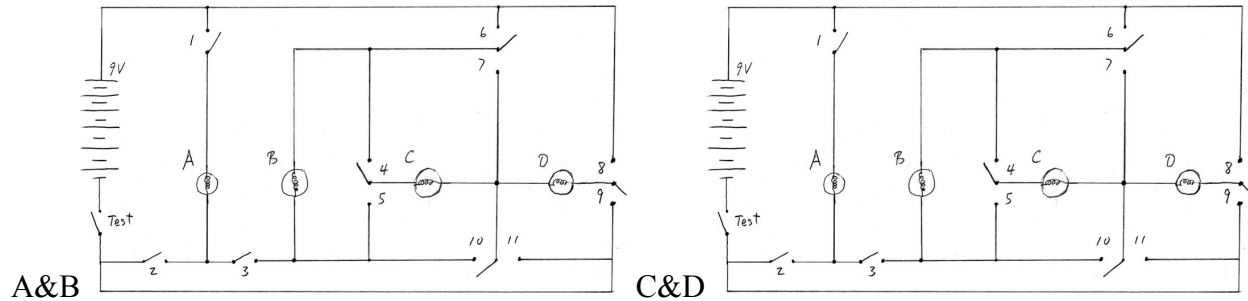
8. On the Foutan schematic, use a colored pencil to show how you would make this circuit using lamp A and B. Next, with C and D.




9. How can you test whether two lamps are in parallel ? _____

10. In parallel, the bulbs should have full brightness, however the power supplies can't supply enough current (they have a high internal resistance). If Dr. H hooks up a stronger power supply, do they achieve full brightness?

 11. Draw a circuit that has a battery, a test switch and **two** light bulbs in **series** and **one** bulb in **parallel with both of them**.



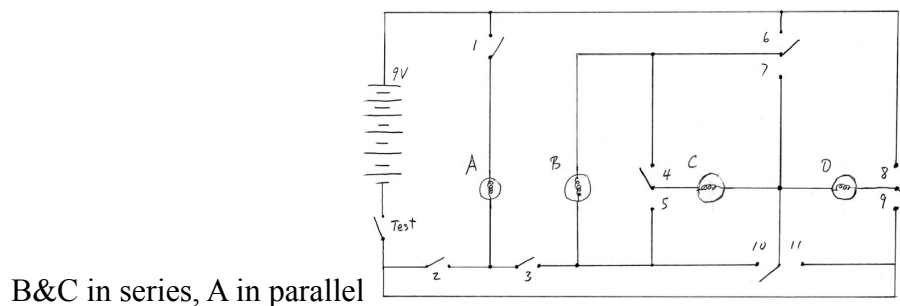12. On the Foutan schematic, use a colored pencil to show how you would make this circuit.



B&C in series, A in parallel

13. What happens when you remove lamp A? _____


14. What happens when you remove lamp B? _____

.....

15. Draw a circuit that has a battery, a test switch and **two** light bulbs in **parallel** and **one** bulb in **series with both of them**.



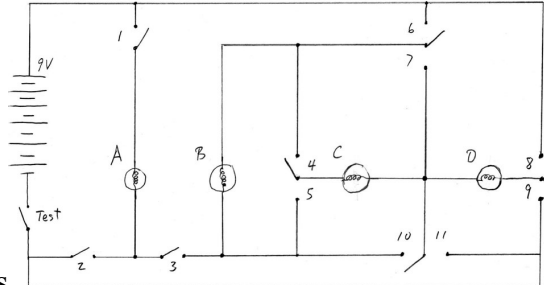16. On the Foutan schematic, use a colored pencil to show how you would make this circuit.





A&B in parallel, C in series

17. What happens when you remove lamp A? _____

18. What happens when you remove lamp C? _____

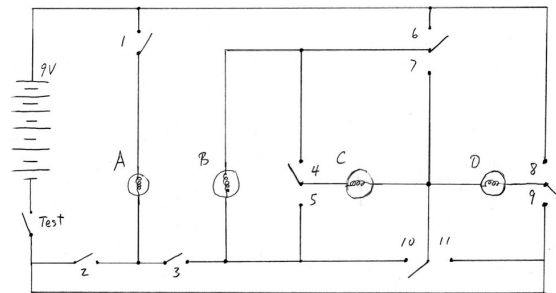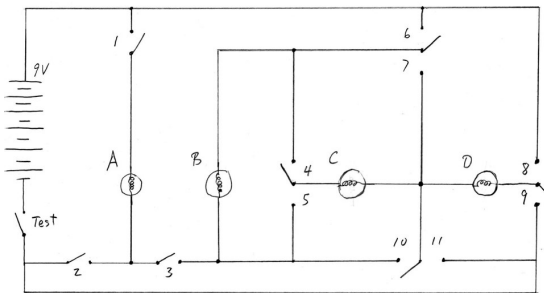19. Extra task. Draw circuit diagram and Foutan setup.



20. Extra task. Draw circuit diagrams and Foutan setup.

